



EE450 - Electronic Control of Motors

Lab 2 - Example 3-9

MATLAB code written by Paco Ellaga

Student ID: 009602331

Course Instructed by Dr. Wajdi Aghnatos

February 12, 2019

Abstract

As per completion of example 3-9 from page 91 of the textbook, *Power Electronics*, by Daniel W. Hart, we were instructed to recreate, complete, and simulate the example using MATLAB.

This example employs the topic of measuring ripple voltage, peak-to-peak voltage variation, capacitance & diode currents. The equations used are from section 3.8, specifically equations 3-37 to 3-51.

MATLAB Code

```
%% Lab 2: Example 3-9
%
clear all, close all, clc;

Vrms = 120;      % volts
f = 60;          % hertz
r = 500;         % ohms
c = 100*10^-6;   % Farads

% Part A: Find the voltage output, Vout
Vm = Vrms*sqrt(2); % volts
W = 377;          % omega
Wrc = W*r*c;      % radians
theta = -atan(Wrc)+pi; % radians
Vtheta = Vm*sin(theta); % volts

Fs = 1000;        % sample frequency
dt = 1/Fs;        % seconds per sample
t = 0:dt:2*pi+theta; % time duration
t1 = 0:dt:2*pi+theta; % time duration (duplicate for fig(2))
```

```

Vout1 = @(t) Vm*sin(t);
Vout2 = @(t) Vtheta*exp(-(t-theta)/Wrc);
Vout1_1 = Vm*sin(t1);
Vout2_1 = Vtheta*exp(-(t1-theta)/Wrc);

% with C = 100uF
figure(1)
subplot(2,2,1)
syms t
Vout = piecewise(0<=t<=theta, Vout1, theta<=t<=(2*pi+theta), Vout2);
fplot(Vout)
grid minor
title('Measurement of Voltage Output where C = 100uF')
legend('Voltage Output where C = 100uF')
xlabel('Frequency'), xlim([0,8])
ylabel('Amplitude'), ylim([-200,200])

% with C = 100uF
subplot(2,2,2)
hold on
plot(t1,Vout1_1)
plot(t1,Vout2_1)
hold off
grid minor
title('Complete measurement of Voltage Output where C = 100uF')
legend('Vout1','Vout2')
xlabel('Frequency'), ylabel('Amplitude')

c1 = 200*10^-6;          % Farads

```

```

Wrc1 = W*r*c1;          % radians
theta1 = -atan(Wrc1)+pi; % radians
Vtheta1 = Vm*sin(theta1); % volts
t3 = 0:dt:2*pi+theta1;   % time duration (duplicate for fig(4))
Vout3 = @(t) Vm*sin(t);
Vout4 = @(t) Vtheta1*exp(-(t-theta1)/Wrc1);
Vout3_1 = Vm*sin(t3);
Vout4_1 = Vtheta1*exp(-(t3-theta1)/Wrc1);

% with C = 200uF
subplot(2,2,3)
syms t
Vout0 = piecewise(0<=t<=theta1, Vout3, theta1<=t<=(2*pi+theta1), Vout4);
fplot(Vout0)
grid minor
title('Measurement of Voltage Output where C = 200uF')
legend('Voltage Output where C = 200uF')
xlabel('Frequency'), xlim([0,8])
ylabel('Amplitude'), ylim([-200,200])

% with C = 200uF
subplot(2,2,4)
hold on
plot(t3,Vout3_1)
plot(t3,Vout4_1)
hold off
grid minor
title('Complete measurement of Voltage Output where C = 200uF')
legend('Vout3','Vout4')

```

```
xlabel('Frequency'), ylabel('Amplitude')
```

```
% Part 2: Find peak-to-peak ripple, Delta Vout
```

```
alpha_fun = @(t) sin(t)-sin(theta)*exp((-2*pi+t-theta)/Wrc);
```

```
alpha = fzero(alpha_fun,0.1);
```

```
deltaVout = Vm*(1-sin(alpha)); % standard answer using equation 3-49
```

```
deltaVout1 = Vm*((2*pi)/(Wrc)); % approximated with equation 3-51
```

```
alpha_funC = @(t) sin(t)-sin(theta1)*exp((-2*pi+t-theta1)/Wrc1);
```

```
alphaC = fzero(alpha_funC,0.1);
```

```
% with C = 200uF
```

```
deltaVout2 = Vm*(1-sin(alphaC)); % standard answer using equation 3-49
```

```
deltaVout3 = Vm*((2*pi)/(Wrc1)); % approximated with equation 3-51
```

```
% Part 3: Find the capacitor current, Ic
```

```
Ic1 = @(t) (-Vtheta/r)*exp(-(t-theta)/Wrc);
```

```
Ic2 = @(t) W*c*Vm*cos(t);
```

```
Ic1_1 = (-Vtheta/r)*exp(-(t1-theta)/Wrc);
```

```
Ic2_1 = W*c*Vm*cos(t1);
```

```
% with C = 100uF
```

```
figure(2)
```

```
subplot(2,2,1)
```

```
syms t
```

```
Vout = piecewise(0<=t<=theta, Ic1, theta<=t<=(2*pi+theta), Ic2);
```

```
fplot(Vout)
```

```
grid minor
```

```

title('Measurement of Capacitor Current where C = 100uF')
legend('Capacitor Current where C = 100uF')
xlabel('Frequency'), xlim([0,8])
ylabel('Amplitude'), ylim([-16,16])

% with C = 100uF
subplot(2,2,2)
hold on
plot(t1,Ic1_1)
plot(t1,Ic2_1)
hold off
grid minor
title('Complete measurement of Capacitor Current where C = 100uF')
legend('Ic1','Ic2')
xlabel('Frequency')
ylabel('Amplitude'), ylim([-16,16])

Ic3 = @(t) (-Vtheta1/r)*exp(-(t-theta1)/Wrc1);
Ic4 = @(t) W*c1*Vm*cos(t);
Ic3_1 = (-Vtheta1/r)*exp(-(t3-theta1)/Wrc1);
Ic4_1 = W*c1*Vm*cos(t3);

% with C = 200uF
subplot(2,2,3)
syms t
Vout00 = piecewise(0<=t<=theta1, Ic3, theta<=t<=(2*pi+theta1), Ic4);
fplot(Vout00)
grid minor
title('Measurement of Capacitor Current where C = 200uF')

```

```

legend('Capacitor Current where C = 200uF')
xlabel('Frequency'), xlim([0,8])
ylabel('Amplitude'), ylim([-16,16])

% with C = 200uF
subplot(2,2,4)
hold on
plot(t3,Ic3_1)
plot(t3,Ic4_1)
hold off
grid minor
title('Complete measurement of Capacitor Current where C = 200uF')
legend('Ic3','Ic4')
xlabel('Frequency')
ylabel('Amplitude'), ylim([-16,16])

% Part 4: Find the peak diode current, Id
% Uses equation 3-48

$$I_d = V_m * (W * c * \cos(\alpha) + (\sin(\alpha)/r));$$
 % peak diode current in amps


$$I_{d1} = V_m * (W * c_1 * \cos(\alpha_C) + (\sin(\alpha_C)/r));$$
 % peak diode current in amps

% Part 5: Find the value of c such that Delta Vout is 1% of Vm
%  $\Delta V_{out} = 0.01 * V_m$ 
% Uses equation 3-51

$$C = V_m / (f * r * (0.01 * V_m));$$
 % Farads

```

Results

1. A expression for the output voltage.

For figure 1 - subplot (2,2,1) and subplot(2,2,2)

$$V_{out3_1} = V_m \sin(t_3);$$

$$V_{out4_1} = V_{\theta 1} \exp(-(t_3 - \theta_1)/W_{rc1});$$

For figure 1 - subplot(2,2,3) and subplot(2,2,4)

$$V_{out0} = \text{piecewise}(0 \leq t \leq \theta_1, V_{out3}, \theta_1 \leq t \leq (2\pi + \theta_1), V_{out4});$$

2. The peak-to-peak voltage variation on the output.

For C= 100uF

$$\Delta V_{out} = V_m (1 - \sin(\alpha)); \quad \% \text{ standard answer using equation 3-49}$$

$$\Delta V_{out1} = V_m ((2\pi)/(W_{rc})); \quad \% \text{ approximated with equation 3-51}$$

```
>> deltaVout
```

```
deltaVout =
```

```
53.7634
```

```
>> deltaVout1
```

```
deltaVout1 =
```

```
56.5672
```

For C = 200uF

$$\Delta V_{out2} = V_m (1 - \sin(\alpha C)); \quad \% \text{ standard answer using equation 3-49}$$

$\Delta V_{out3} = V_m * ((2 * \pi) / (W * r * C_1));$ % approximated with equation 3-51

```
>> deltaVout2

deltaVout2 =

    28.4214

>> deltaVout3

deltaVout3 =

    28.2836
```

3. An expression for the capacitor current.

For figure 2 - subplot (2,2,1) and subplot(2,2,2)

$I_{c1_1} = (-V_{\theta} / r) * \exp(-(t_1 - \theta) / W * r * C_1);$

$I_{c2_1} = W * C_1 * V_m * \cos(t_1);$

For figure 1 - subplot (2,2,3) and subplot(2,2,4)

$I_{cOut0} = \text{piecewise}(0 \leq t \leq \theta_1, I_{c3}, \theta_1 \leq t \leq (2 * \pi + \theta_1), I_{c4});$

4. Power the peak diode current.

For $C = 100 \mu F$

$I_d = V_m * (W * C_1 * \cos(\alpha) + (\sin(\alpha) / r));$ % peak diode current in amps

For $C = 200 \mu F$

$I_{d1} = V_m * (W * C_1 * \cos(\alpha_C) + (\sin(\alpha_C) / r));$ % peak diode current in amps

```
>> Id

Id =

    4.9039

>> Id1

Id1 =

    7.3713
```

5. The value of such ΔC such that V_o is 1 percent of V_m .

$$C = V_m / (f * r * (0.01 * V_m)); \quad \% \text{ Farads}$$

```
>> C

C =

    0.0033
```

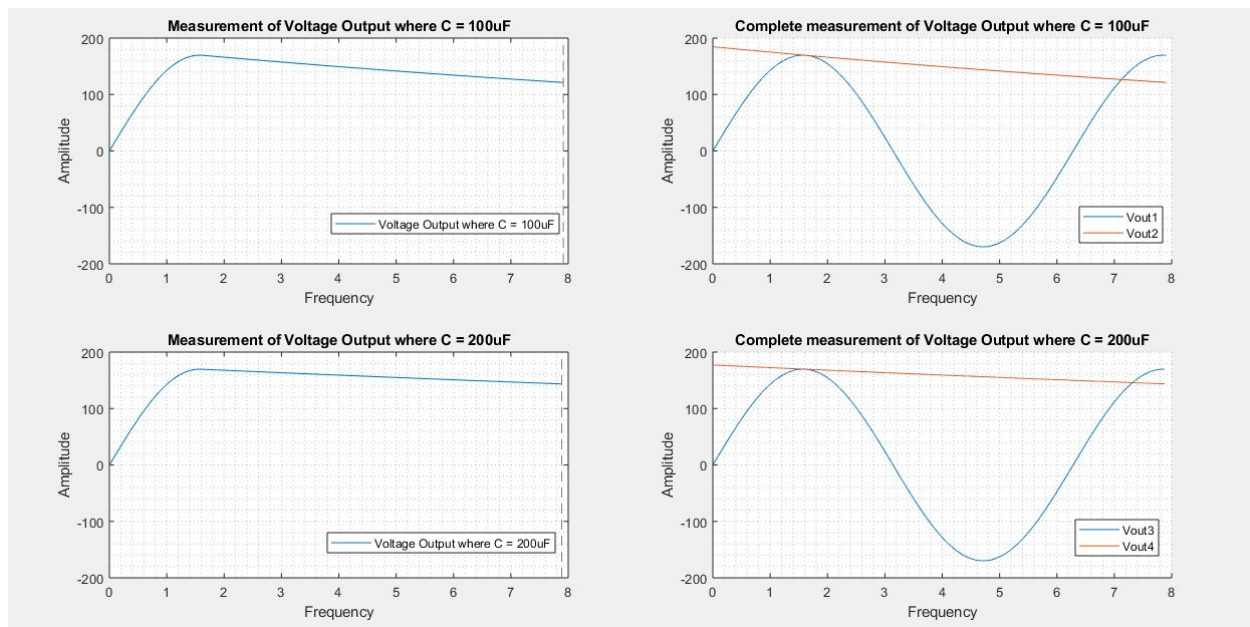


Figure 1: Representation of the peak-to-peak voltage variation on the output

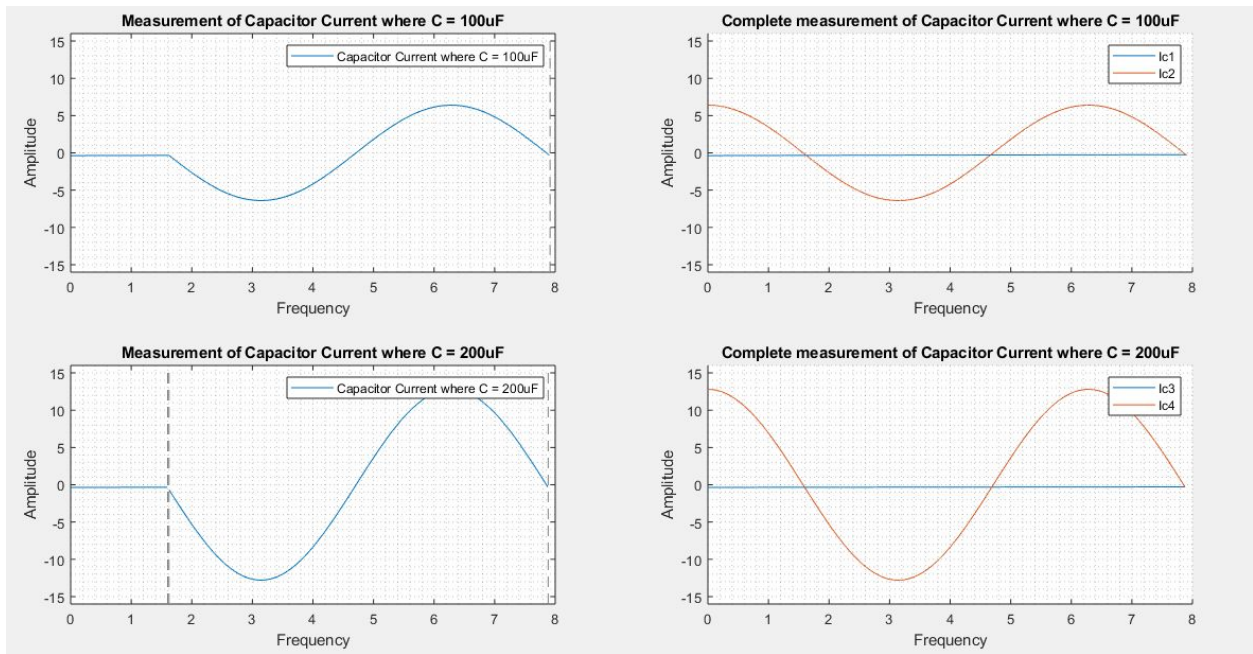


Figure 2: Representation of the expression for the capacitor current

Conclusion

In result of the example and change of the capacitor value, there is a slight change in both the current of the capacitor and the peak-to-peak voltage output. When changed from $100\mu\text{F}$ to $200\mu\text{F}$, the drop-off of the output over time decays slower due to increased capacitance being directly inflicted on multiple parts of the system. As for the capacitor's current, the increase of micro-Farads increases the amplitude showing a higher and stronger peak current capacity. When the value of the capacitor is adjusted to be Delta V_{out} 's 1% of the V_m , the value of the capacitor will raise up due to the optimization of the V_m being compared to the peak to peak voltage.